


Types of Circuits

Series and Parallel Circuits


Mr. Duke

A Series Circuit

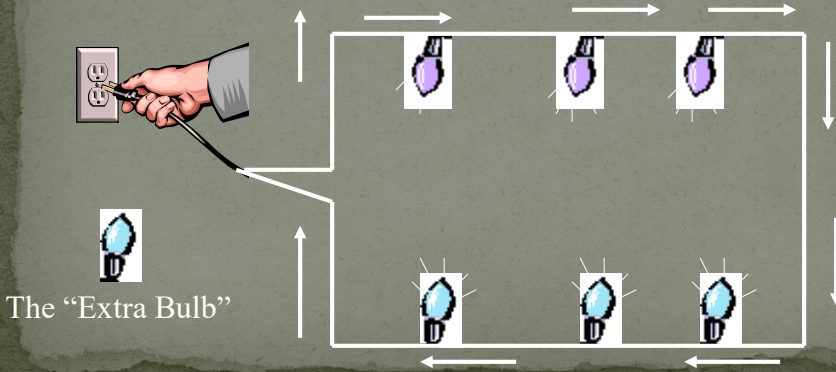Only ONE pathway from negative to positive
If one light bulb burns out the rest will not work



Current in a Series Circuit

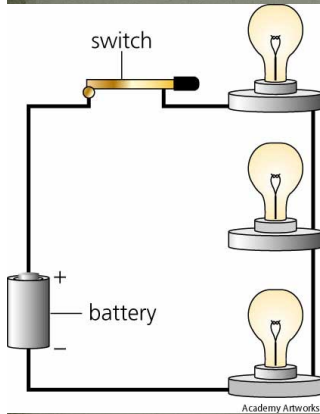

Current only has 1 path to follow, so it must flow through each part of the circuit.

$$I_T = I_1 = I_2 = I_3 = \dots$$


Charge can't be created or destroyed, so

current is constant throughout the circuit


Resistance in a Series Circuit

Total Resistance = sum of individual resistances

$$R_T = R_1 + R_2 + R_3 + \dots$$

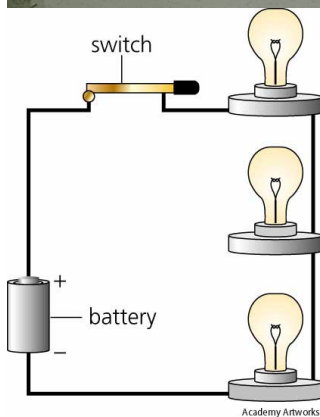

Voltage in a Series Circuit

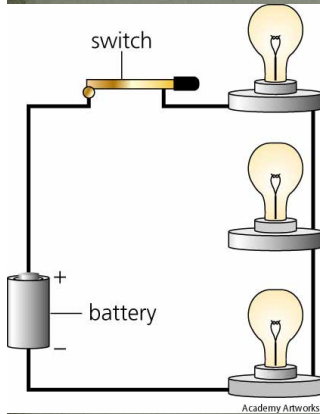

$$V_{\text{total}} = V_{\text{drop}}$$

$$\text{Voltage drop} = V_T = V_1 + V_2 + V_3 + \dots$$

$$V = I \times R \quad \text{Ohm's Law}$$

Series Circuit Equations

$$I = \text{constant}$$


$$R_{\text{total}} = R_1 + R_2 + R_3$$

$$V_{\text{total}} = V_1 + V_2 + V_3$$


Voltmeters and Ammeters placement

Voltmeters are placed across the resistor

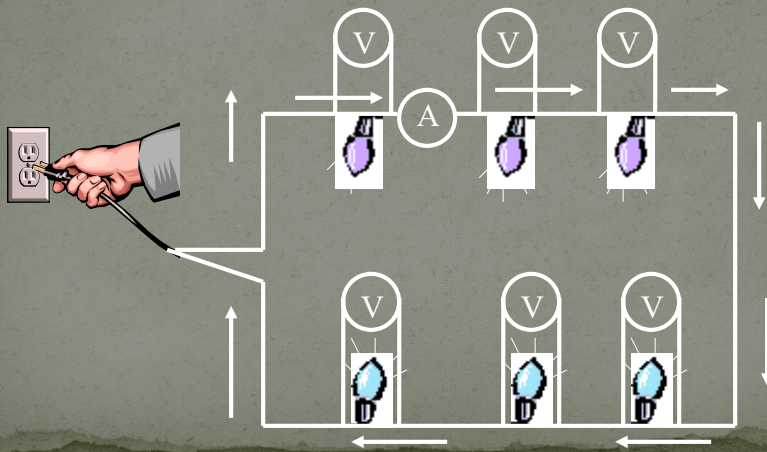Ammeters are placed in series with the resistor



Example

Resistors in series  2C, 6E

1. A 12.0 V storage battery is connected to three resistors, 6.75 Ω , 15.3 Ω , and 21.6 Ω , respectively. The resistors are joined in series.
 - a. Calculate the equivalent resistance.
 - b. What is the current in the circuit?

Example

- 2.** A $4.0\ \Omega$ resistor, an $8.0\ \Omega$ resistor, and a $12.0\ \Omega$ resistor are connected in series with a $24.0\ \text{V}$ battery.
- Calculate the equivalent resistance.
 - Calculate the current in the circuit.
 - What is the current in each resistor?

Example

- 4.** A series combination of two resistors, $7.25\ \Omega$ and $4.03\ \Omega$, is connected to a $9.00\ \text{V}$ battery.
- Calculate the equivalent resistance of the circuit and the current.
 - What is the potential difference across each resistor?

Example


5. A $7.0\ \Omega$ resistor is connected in series with another resistor and a $4.5\ \text{V}$ battery. The current in the circuit is $0.60\ \text{A}$. Calculate the value of the unknown resistance.

Example

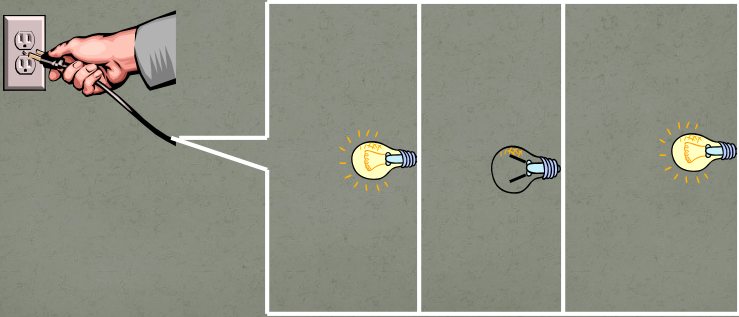6. Several light bulbs are connected in series across a $115\ \text{V}$ source of emf.
- What is the equivalent resistance if the current in the circuit is $1.70\ \text{A}$?
 - If each light bulb has a resistance of $1.50\ \Omega$, how many light bulbs are in the circuit?


A Parallel Circuit

More than ONE pathway from negative to positive
If one light bulb burns out it will not affect the rest



A Parallel Circuit

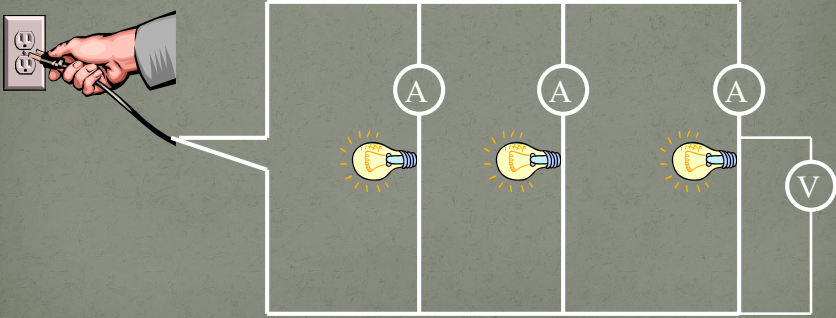The voltage across each parallel branch is the same.
To measure the current you will need an Ammeter in each branch.



$V = I \times R$ Ohm's Law

Parallel Circuit Equations

$$I_T = I_1 + I_2 + I_3$$

$$1/R_{\text{total}} = 1/R_1 + 1/R_2 + 1/R_3$$

$$V_{\text{total}} = V_1 = V_2 = V_3$$

Example Problems done in class

2. A length of wire is cut into five equal pieces. The five pieces are then connected in parallel, with the resulting resistance being 2.00Ω . What was the resistance of the original length of wire before it was cut up?

Example Problems done in class

3. A $4.0\ \Omega$ resistor, an $8.0\ \Omega$ resistor, and a $12.0\ \Omega$ resistor are connected in parallel across a $24.0\ \text{V}$ battery.
- What is the equivalent resistance of the circuit?
 - What is the current in each resistor?

Example Problems done in class

4. An $18.0\ \Omega$, $9.00\ \Omega$, and $6.00\ \Omega$ resistor are connected in parallel to an emf source. A current of $4.00\ \text{A}$ is in the $9.00\ \Omega$ resistor.
- Calculate the equivalent resistance of the circuit.
 - What is the potential difference across the source?
 - Calculate the current in the other resistors.